

به نام خدا

حافظه‌ها


نگاشت حافظه

Dr. Aref Karimafshar
A.karimafshar@ec.iut.ac.ir




کنار هم قرار دادن سلول‌های حافظه

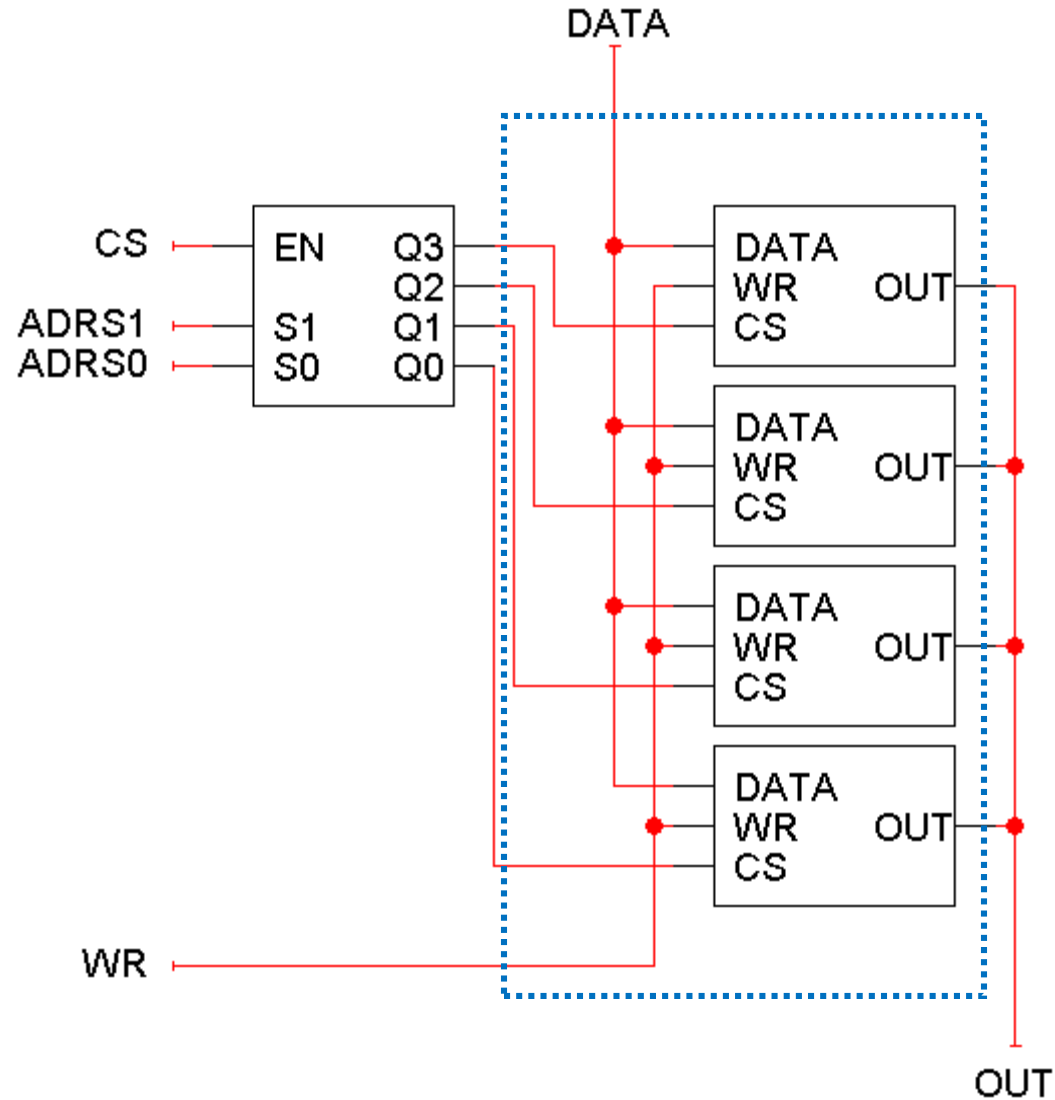- Here is the 4 x 1 RAM once again.
- How can we make a “wider” memory with more bits per word, like maybe a 4 x 4 RAM?
- Duplicate the stuff in the blue box!



A 4 x 4 RAM

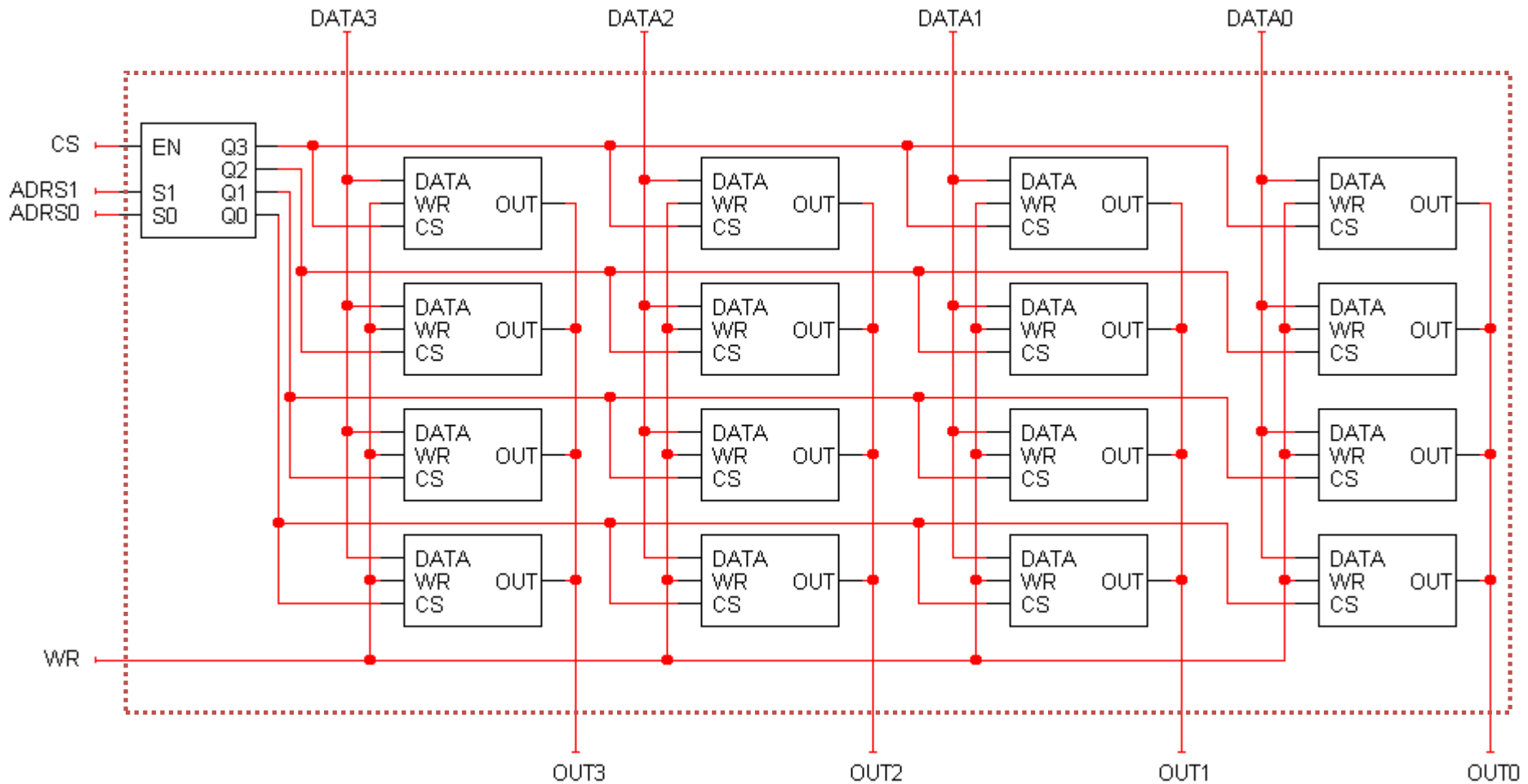DATA and OUT are now each *four* bits long, so you can read and write four-bit words.




توسعه حافظه

- Available memory can be expanded
 - To increase the word length
 - Number of bits in each address
 - To increase the word capacity
 - Number of different addresses
- Memory expansion is accomplished by
 - Adding an appropriate number of memory chips to
 - Address buses
 - Data buses
 - Control buses


Increase the Word Length

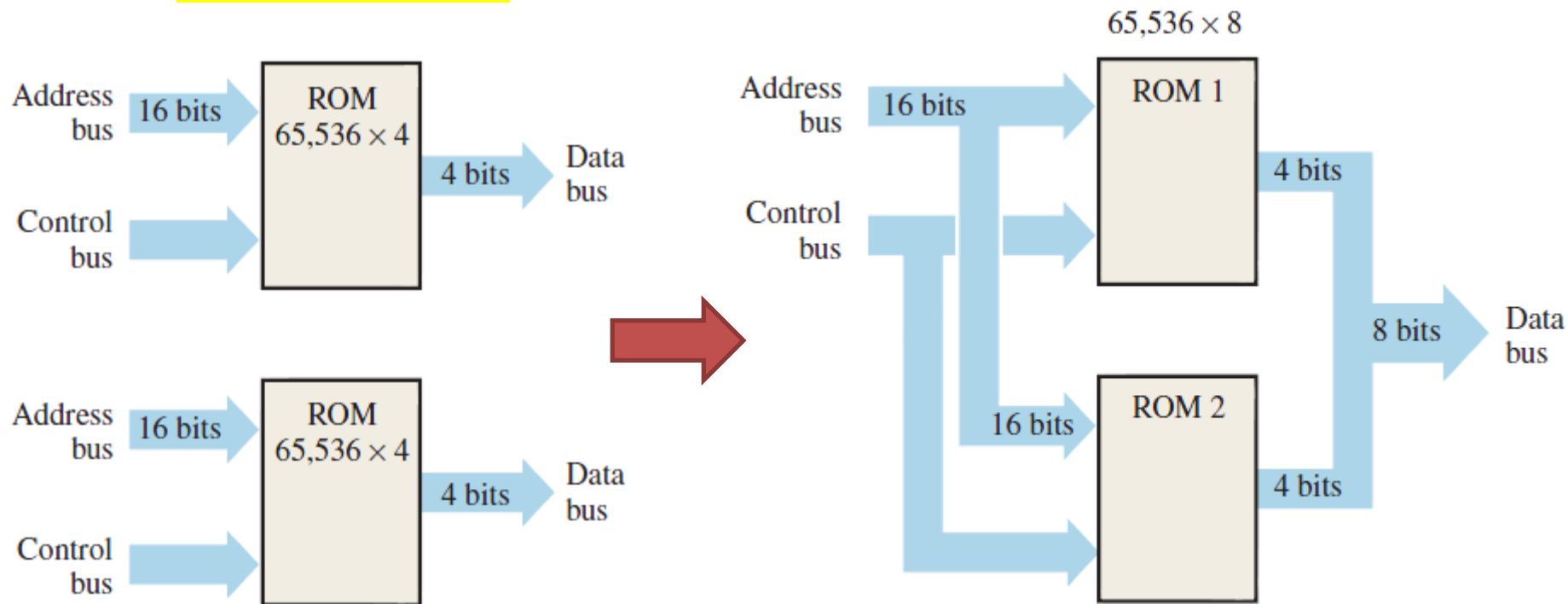- Number of bits in **data bus** must be increased
- For example
 - 8-bit word length can be achieved by using **two memories, each with 4-bit words**




مثال

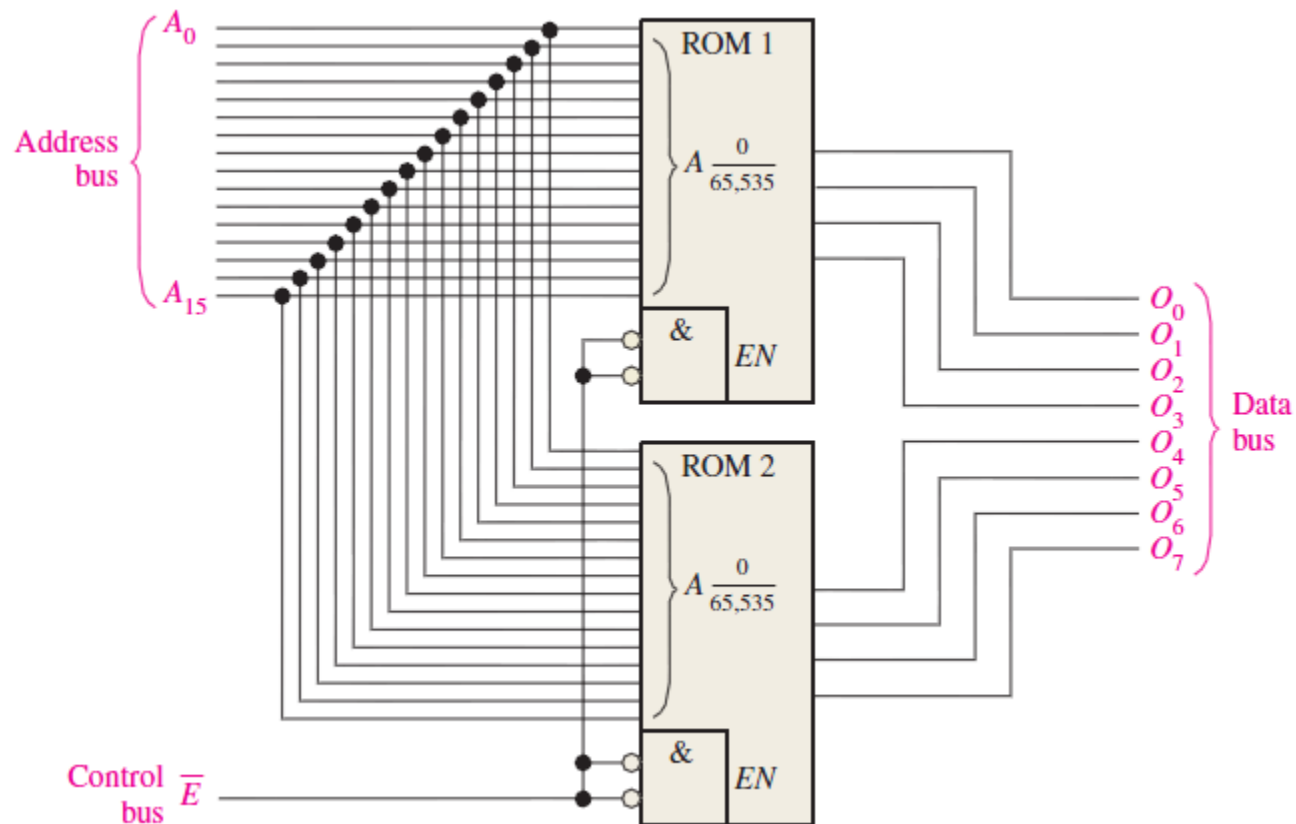توسعه دو حافظه ROM 64k×4 برای تشکیل یک حافظه ROM 64k×8



مثال

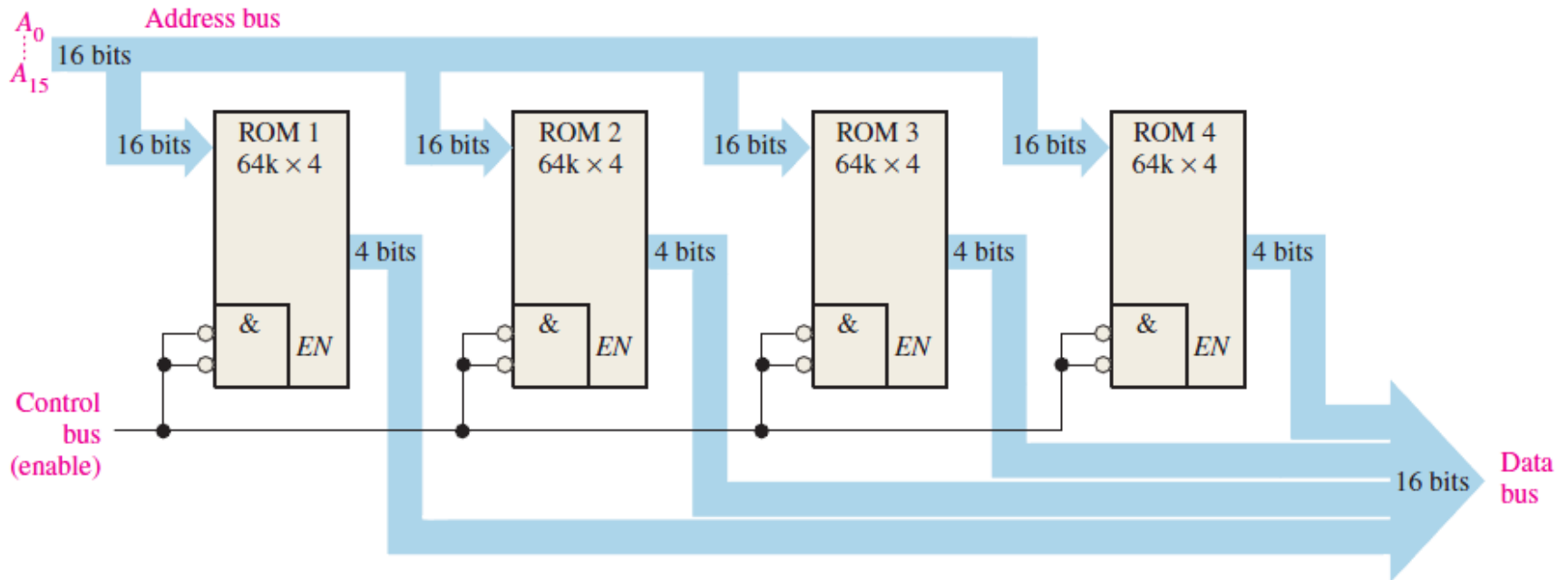
تشکیل یک حافظه $64k \times 16$ ROM با استفاده از چهار حافظه $64k \times 4$ ROM



Word-length Expansion in a RAM


Design a 64K x 16 RAM, using two 64K x 8 chips.

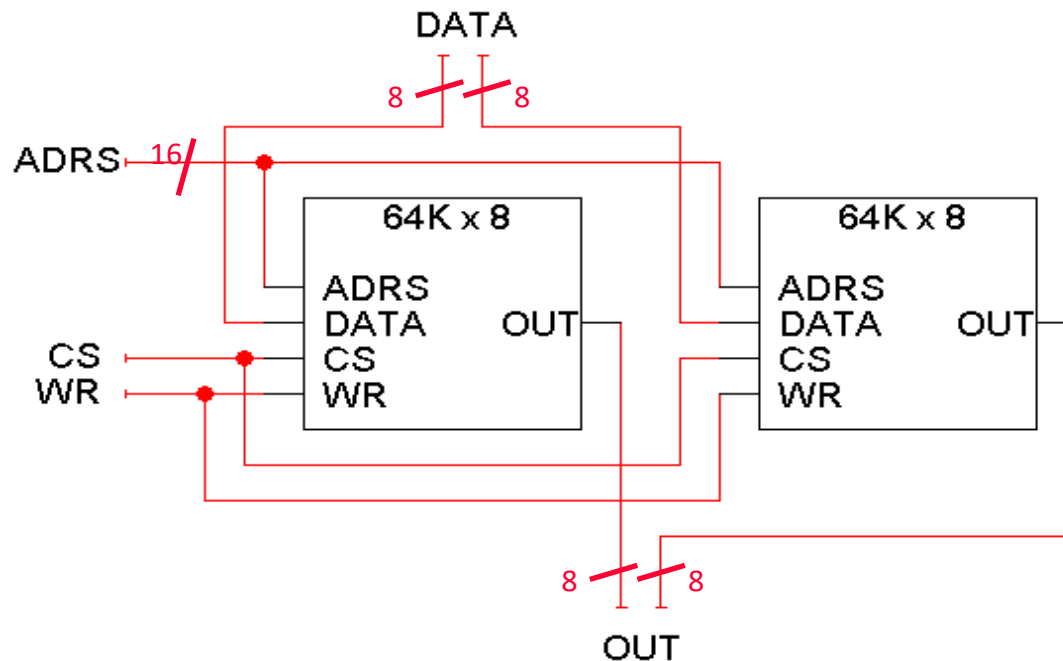- The left chip contains the most significant 8 bits of the data.
- The right chip contains the lower 8 bits of the data.




Word-length Expansion in a RAM

Tri-state buffers are required

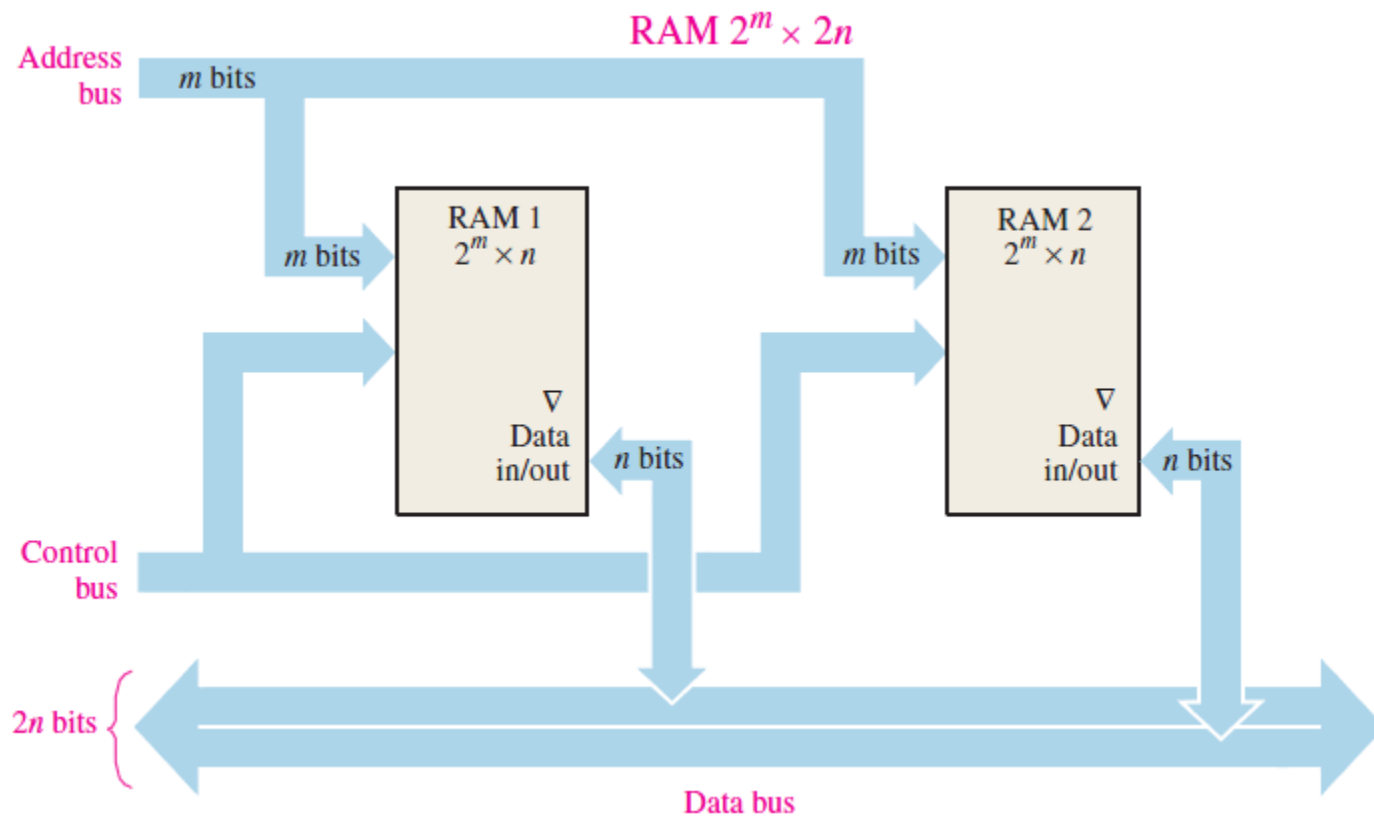


مثال

1M × 4 SRAMs to create a 1M × 8 SRAM

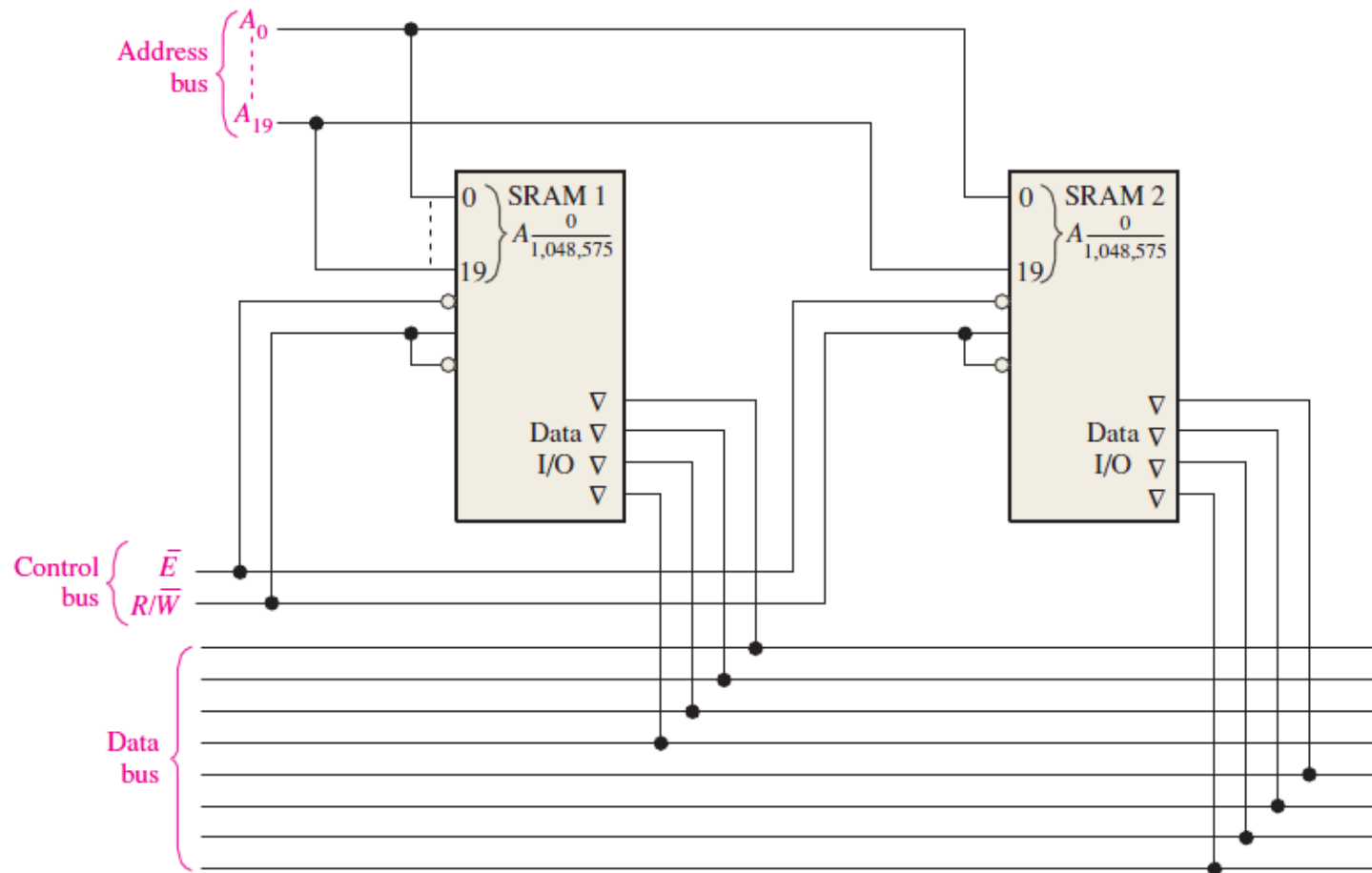


Word-Capacity Expansion

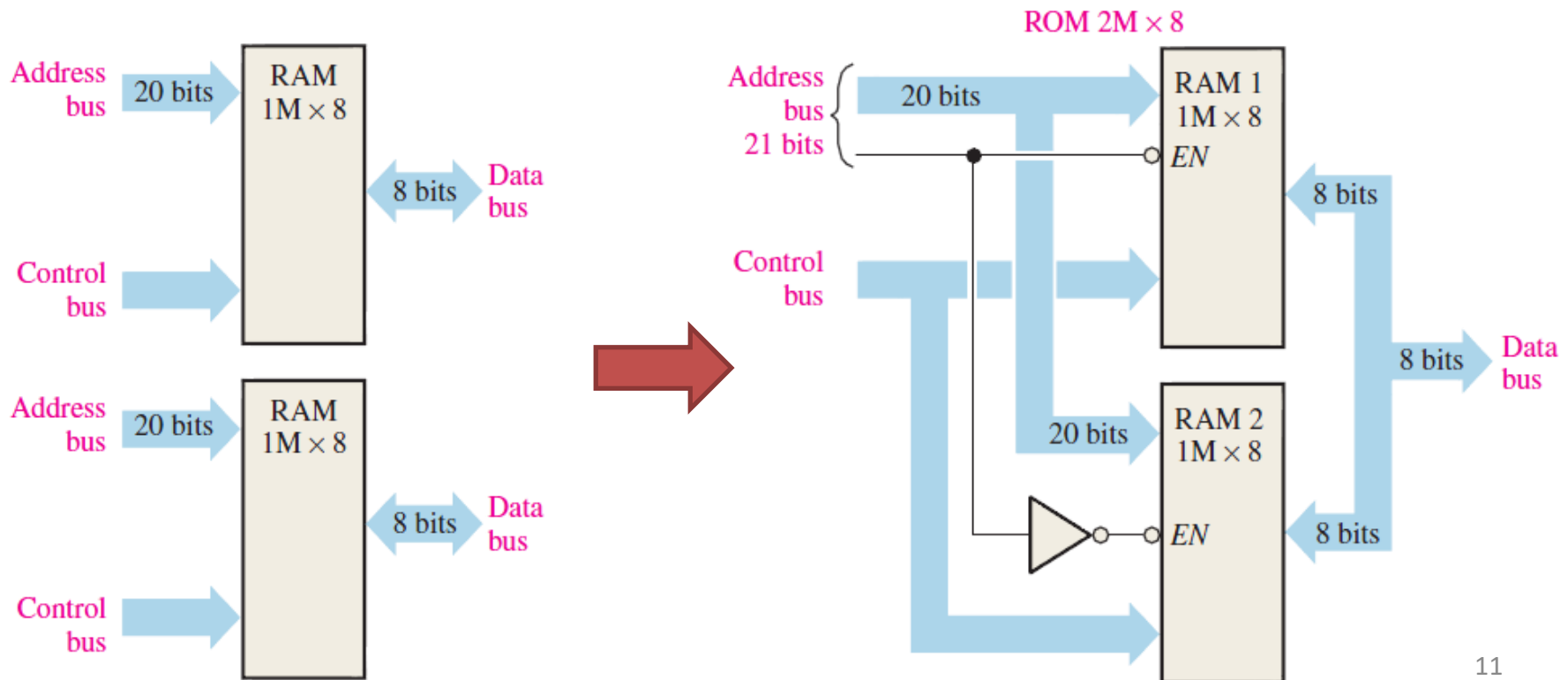- Number of **address bits** must be increased
- For example
 - Two $1\text{M} \times 8$ RAMs are expanded to form a $2\text{M} \times 8$ memory



مثال

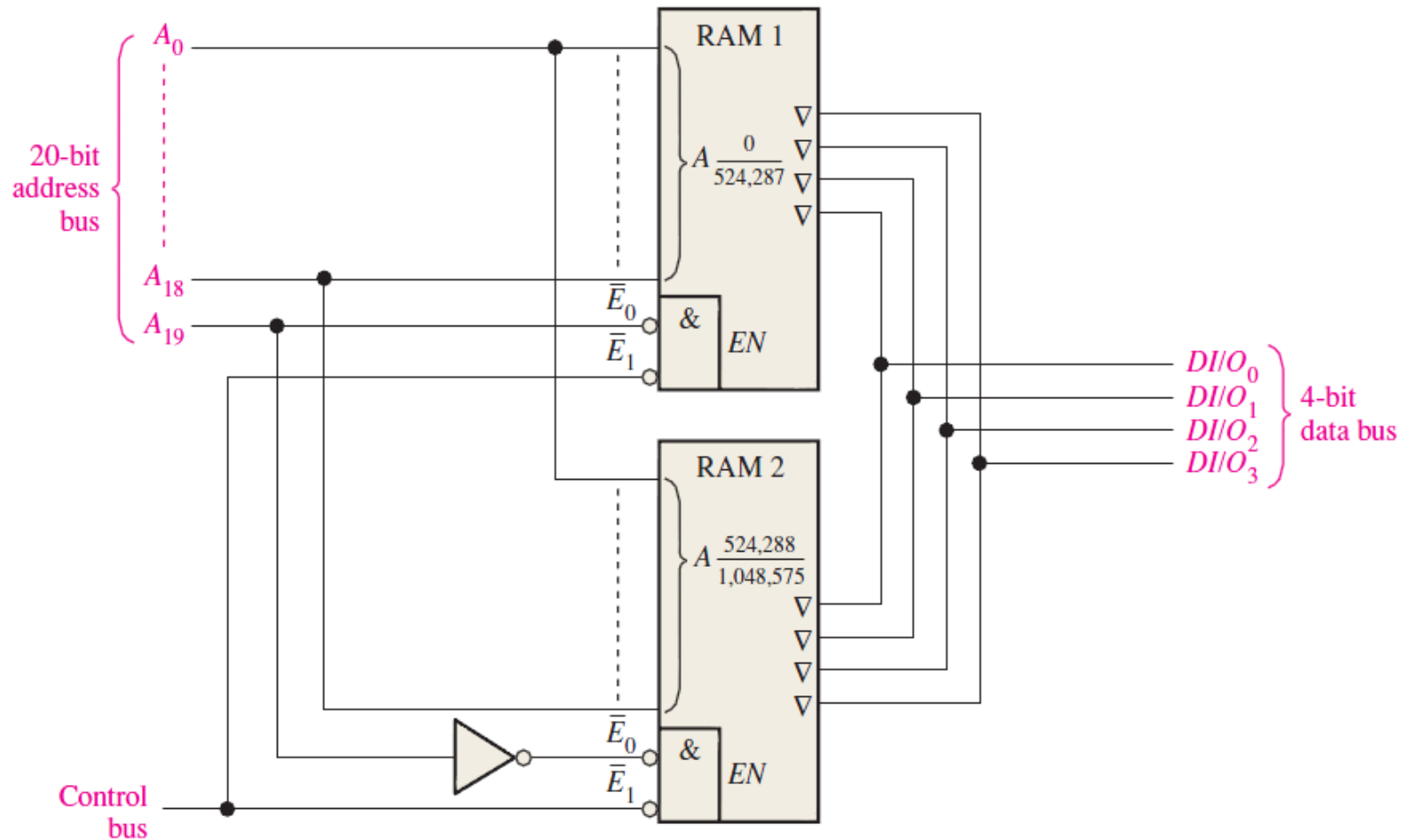512k × 4 RAMs to implement a 1M × 4 memory




Making a larger memory

Example

Design a **256K x 8** memory, given that you have **64K x 8** chips


Solution

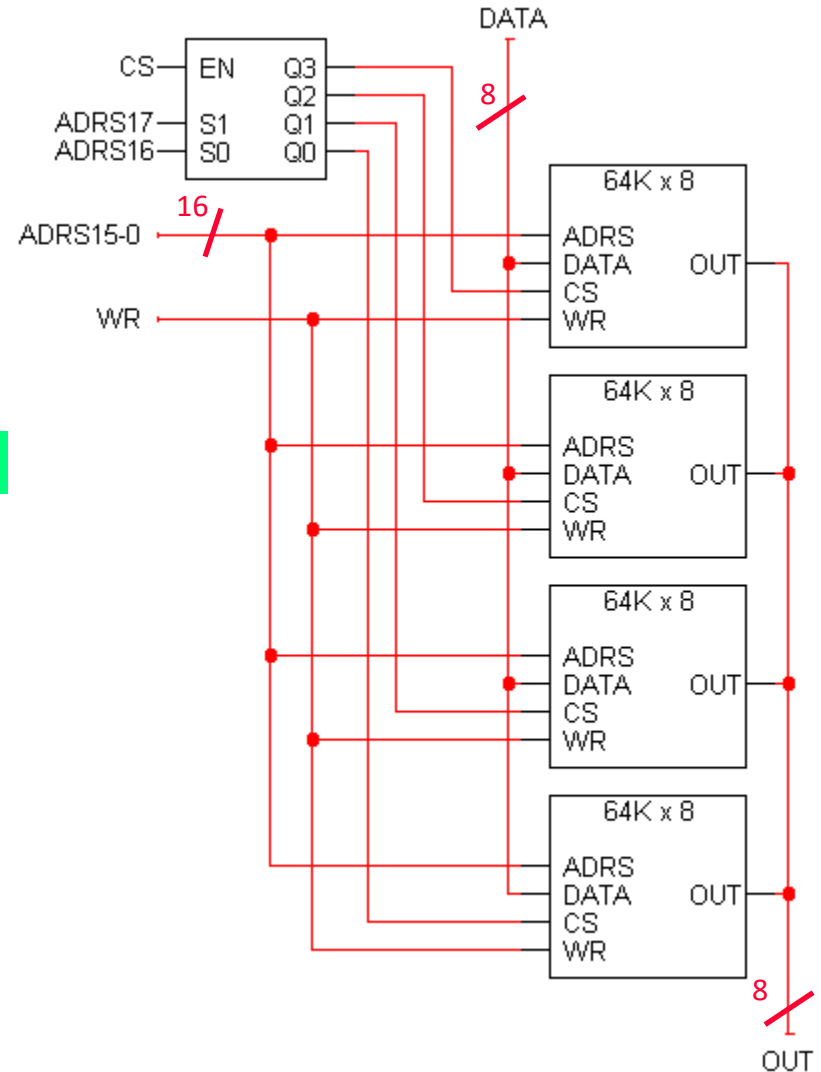- For **256K words**, we **need 18 address lines**.
 - The **two most significant address lines** go to the **decoder**, which selects **one of the four 64K x 8 RAM chips**.
 - The other 16 address lines are shared by the 64K x 8 chips.
- The 64K x 8 chips also **share WR** and **DATA** inputs.
- This assumes the 64K x 8 chips have **three-state outputs**.




Analyzing the 256K x 8 RAM

- There are 256K words of memory, spread out among the four smaller 64K x 8 RAM chips.
- When the two most significant bits of the address are 00, the bottom RAM chip is selected. It holds data for the first 64K addresses.
- The next chip up is enabled when the address starts with 01. It holds data for the second 64K addresses.
- The third chip up holds data for the next 64K addresses.
- The final chip contains the data of the final 64K addresses.

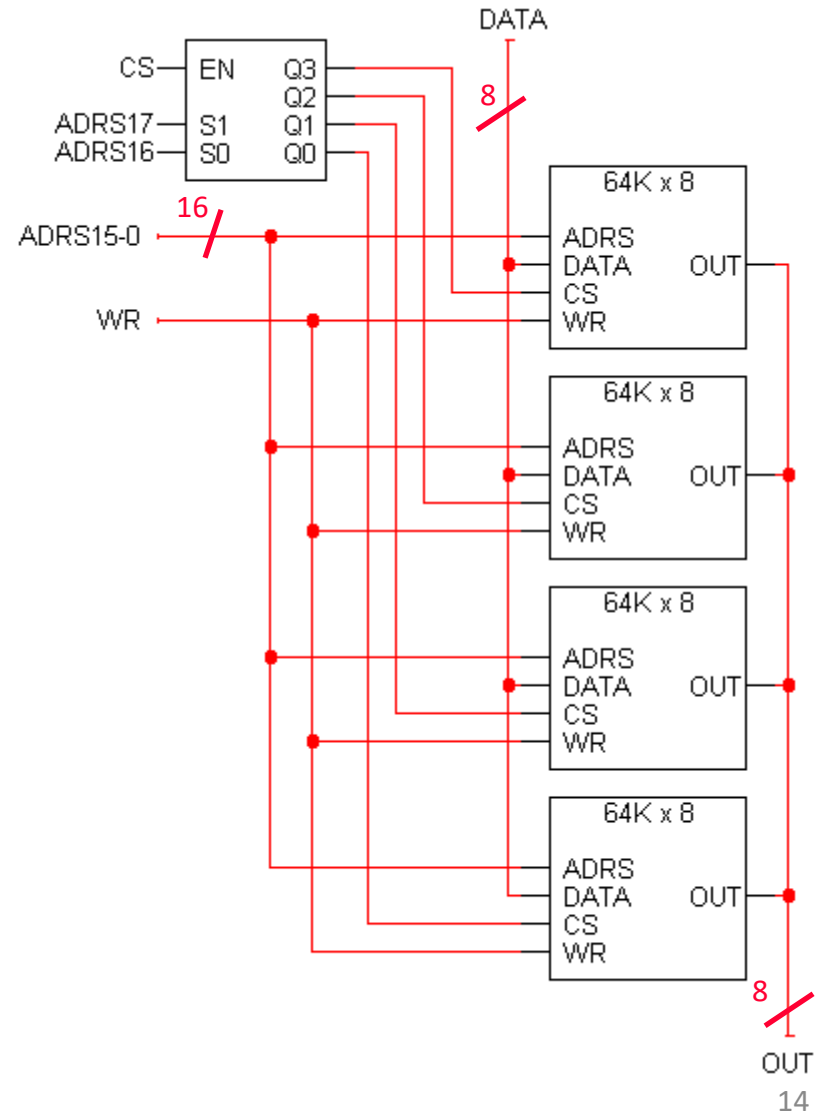


Address ranges

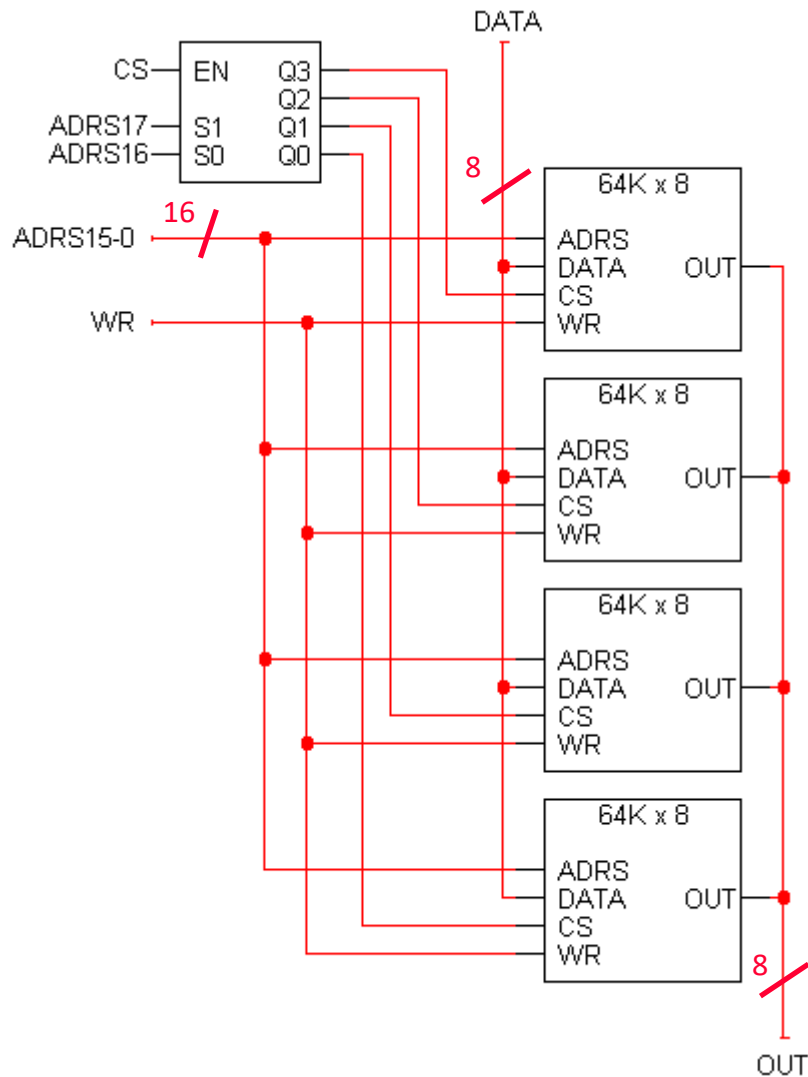

11	1111	1111	1111	1111	(0x3ffff)
to					
11	0000	0000	0000	0000	(0x30000)
to					
10	1111	1111	1111	1111	(0x2ffff)
to					
10	0000	0000	0000	0000	(0x20000)
to					
01	1111	1111	1111	1111	(0x1ffff)
to					
01	0000	0000	0000	0000	(0x10000)
to					
00	1111	1111	1111	1111	(0x0ffff)
to					
00	0000	0000	0000	0000	(0x00000)


ماژول‌های حافظه

- Memory module
 - A narrow printed circuit board that holds memory chips
- Memory module types
 - Single In-Line Memory Module (SIMM)
 - Widely used from the late 1980s to 1990s
 - Typically had 32-bit data bus
 - Available in two physical types—30- and 72-pin
 - Dual In-Line Memory Module (DIMM)
 - "Dual in-line" refers to pins on both sides of the modules
 - Originally had a 168-pin connector supporting 64-bit data bus
 - which is twice the data width of SIMMs

 

SIMM

 - 72-pin SIMM - use a data path of 32 bits




SIMM

- 30-pin SIMM- use a 16-bit address bus




DIMM

- 168-pin SDRAM DIMM

 

DIMM

 - 184-pin DDR DIMM
 - DDR SDRAM performs two transfers per clock cycle




Key Features

 - 133.35mm x 30.48 mm
- 184 pins
- 2.5V
- Registered/Unbuffered
- x 64 / x 72
- MO-206


DIMM

- 240-pin **DDR2 DIMM**
 - Successor to DDR SDRAM
 - Features a **four-bit prefetch buffer**
 - Enabling faster performance, however has **greater latency than DDR SDRAM**



DIMM

 - 240-pin DDR3 DIMM
 - Compared to DDR2, DDR3 runs at lower voltages
 - Most versions run at faster speeds than DDR2
 - Has an eight-bit prefetch bus
 - As with DDR2 versus DDR, DDR3 has greater latency than DDR2



Key Features

- 133.35mm x 30mm
- 240 pins
- 1.5V / 1.35V (LRDIMM)
- Registered/Unbuffered
- x 64 / x 72
- MO-269

DIMM



Reduced-size memory modules known as small outline DIMMs (SO-DIMMs or SODIMMs)

 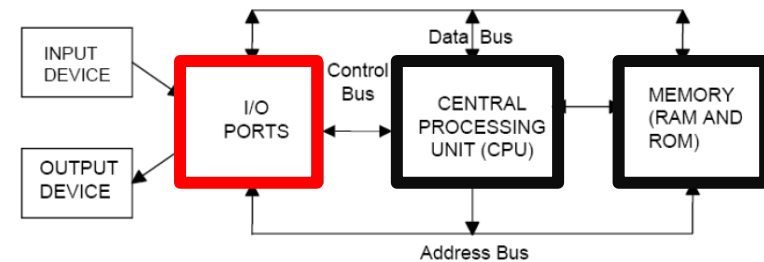- 1.DDR2 SO-DIMM
- 2.DDR2 DIMM
- 3.DDR3 SO-DIMM
- 4.DDR3 DIMM




I/O Subsystem

- Provides the mechanism for communication between CPU and outside world
- Manages communications
 - Asynchronous with respect the CPU
 - Have widely ranging data rates



ساختار گذرگاه I/O

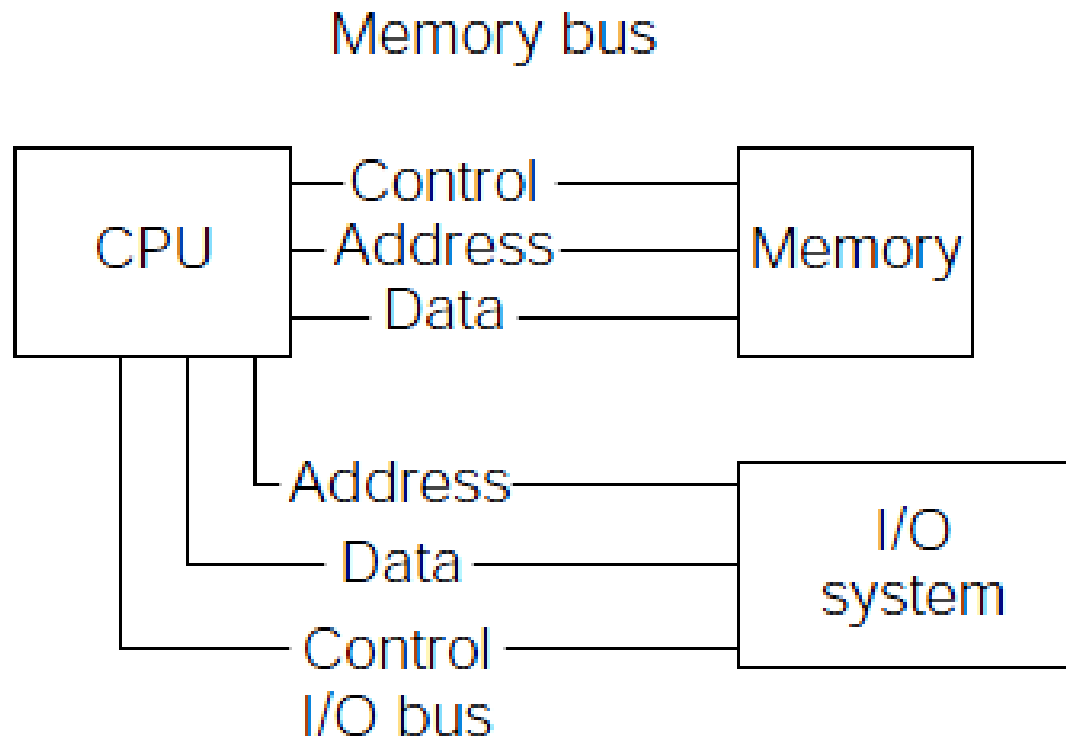


Separate memory and I/O buses



Isolated I/O

ساختار گذرگاه I/O

 


Shared address and data lines



Shared I/O

ساختار گذرگاه I/O

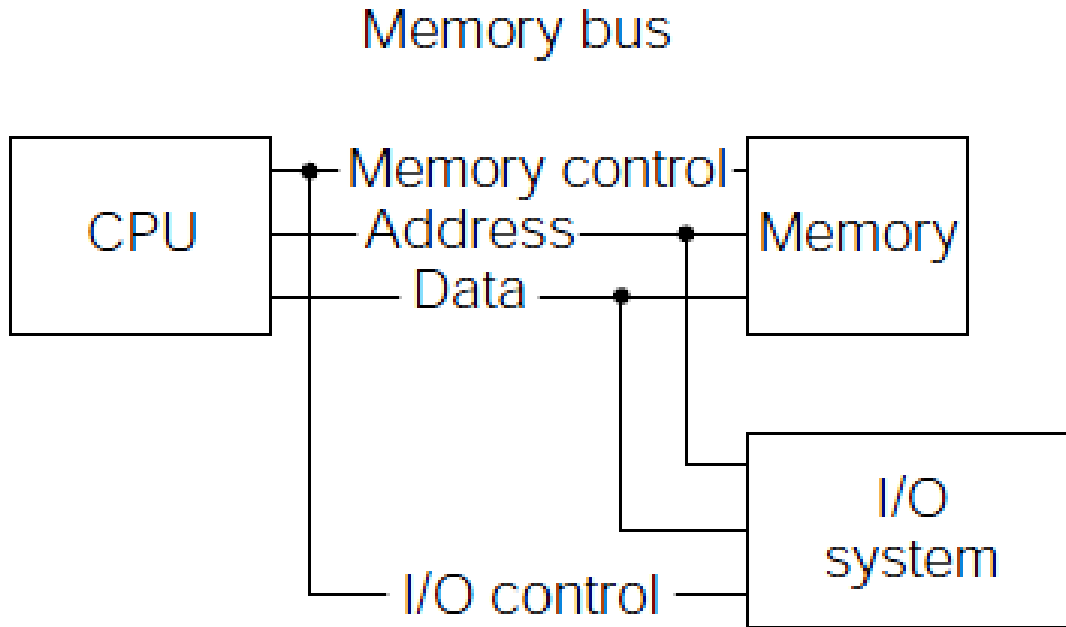

Shared address, data, and control lines




memory-mapped I/O


Memory Mapped I/O

- Combine memory control and I/O control lines to make one unified bus for memory and I/O
- This makes addresses of I/O device registers appear to the processor as memory addresses
- Reduces the number of connections to the processor chip
- Standardizes data transfer to and from the processor


Memory Mapped I/O

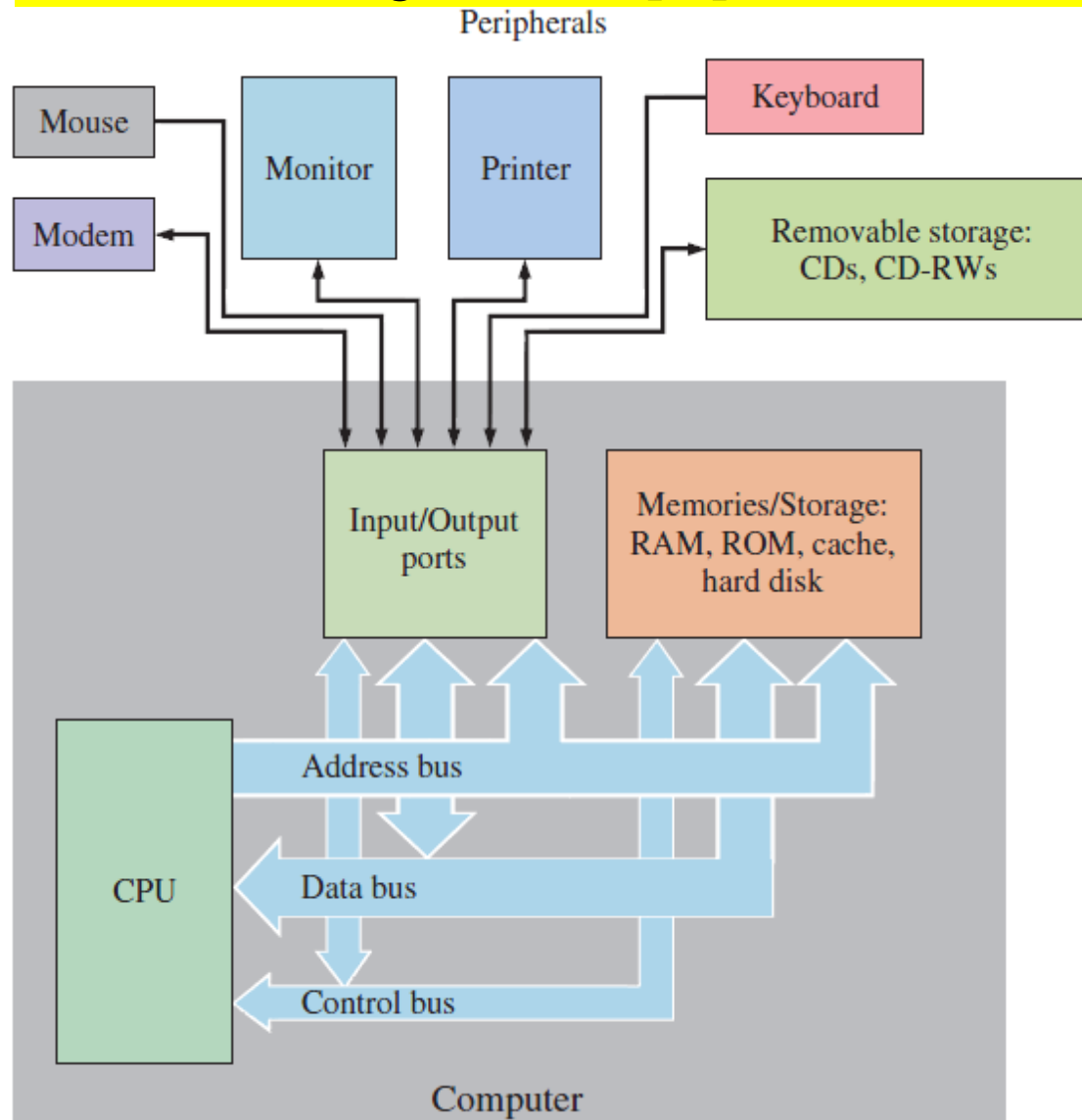

Memory Mapped I/O

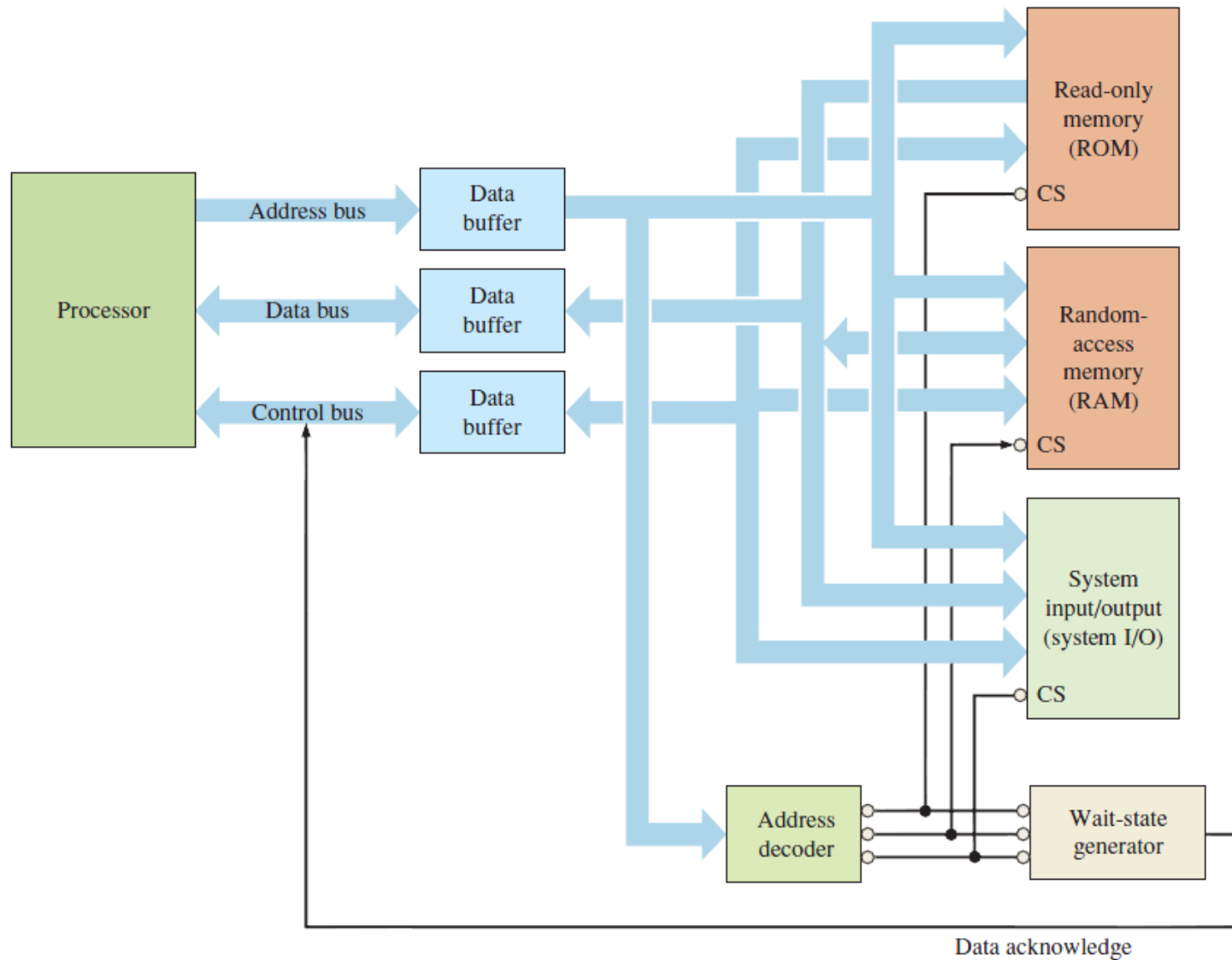

Address Space (using Memory Mapped I/O)

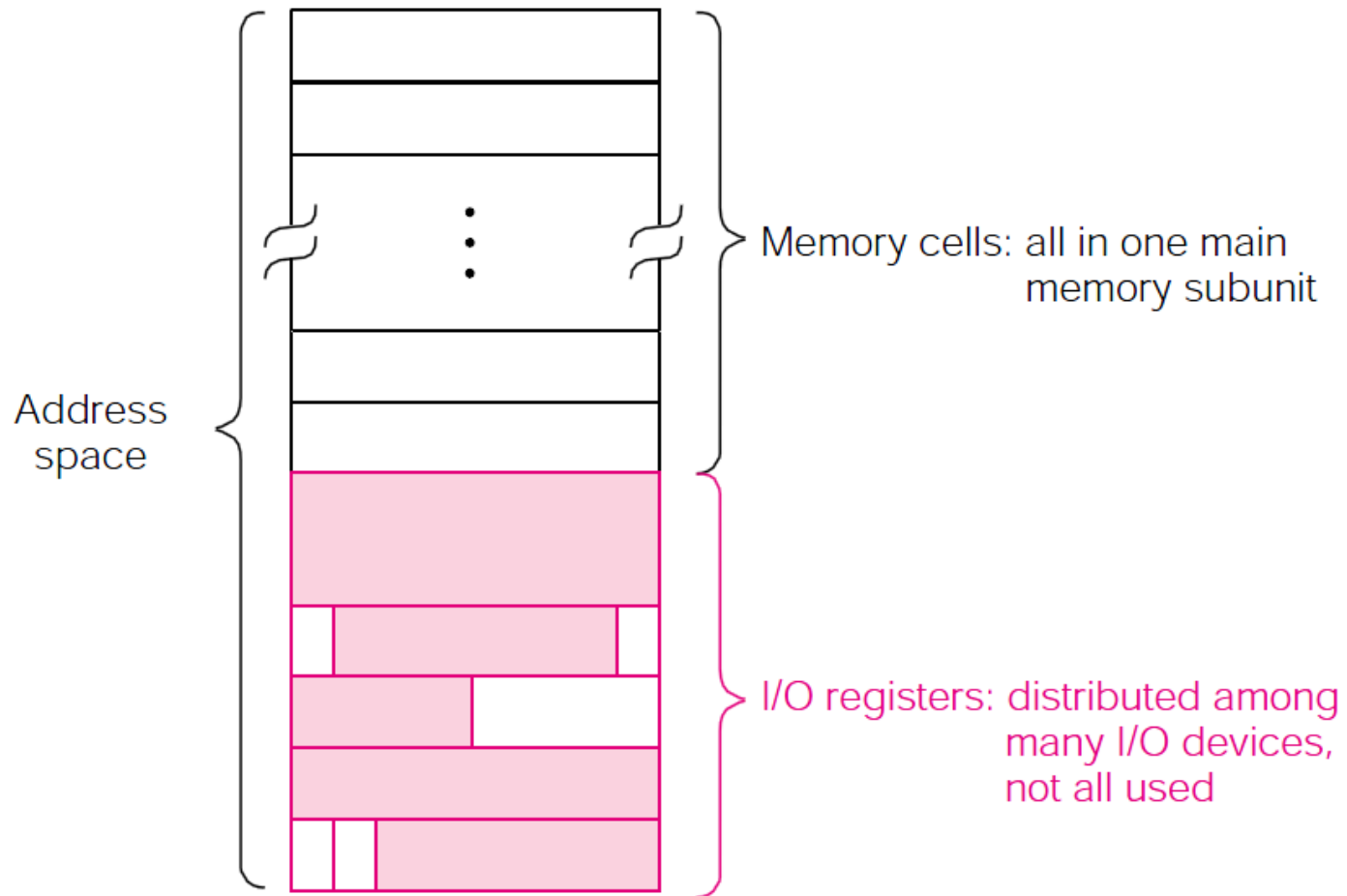


Programmed I/O

Device Interface Structure

- Processor must know when output device can accept new data
- Processor must know when input device is ready to supply new data
- Synchronization can be done by processor reading device status bits
 - Data available signal from input device
 - Ready to accept output data from output device
- Example status bits:
 - Input data ready
 - Output device busy or off-line
- Example control bits:
 - Reset device
 - Start read or start write


Programmed I/O

Device Interface Structure

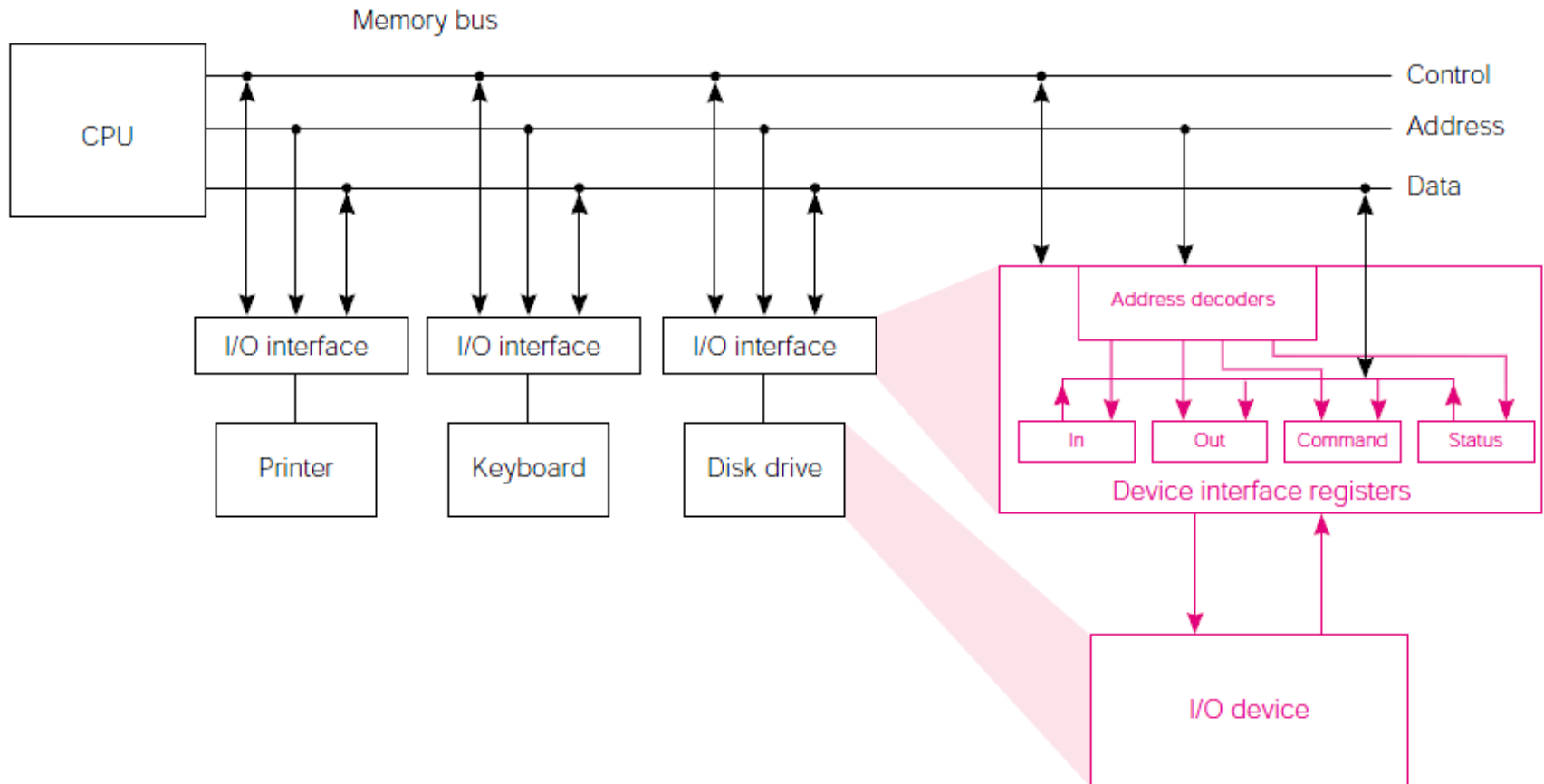

Programmed I/O

Device Interface Structure

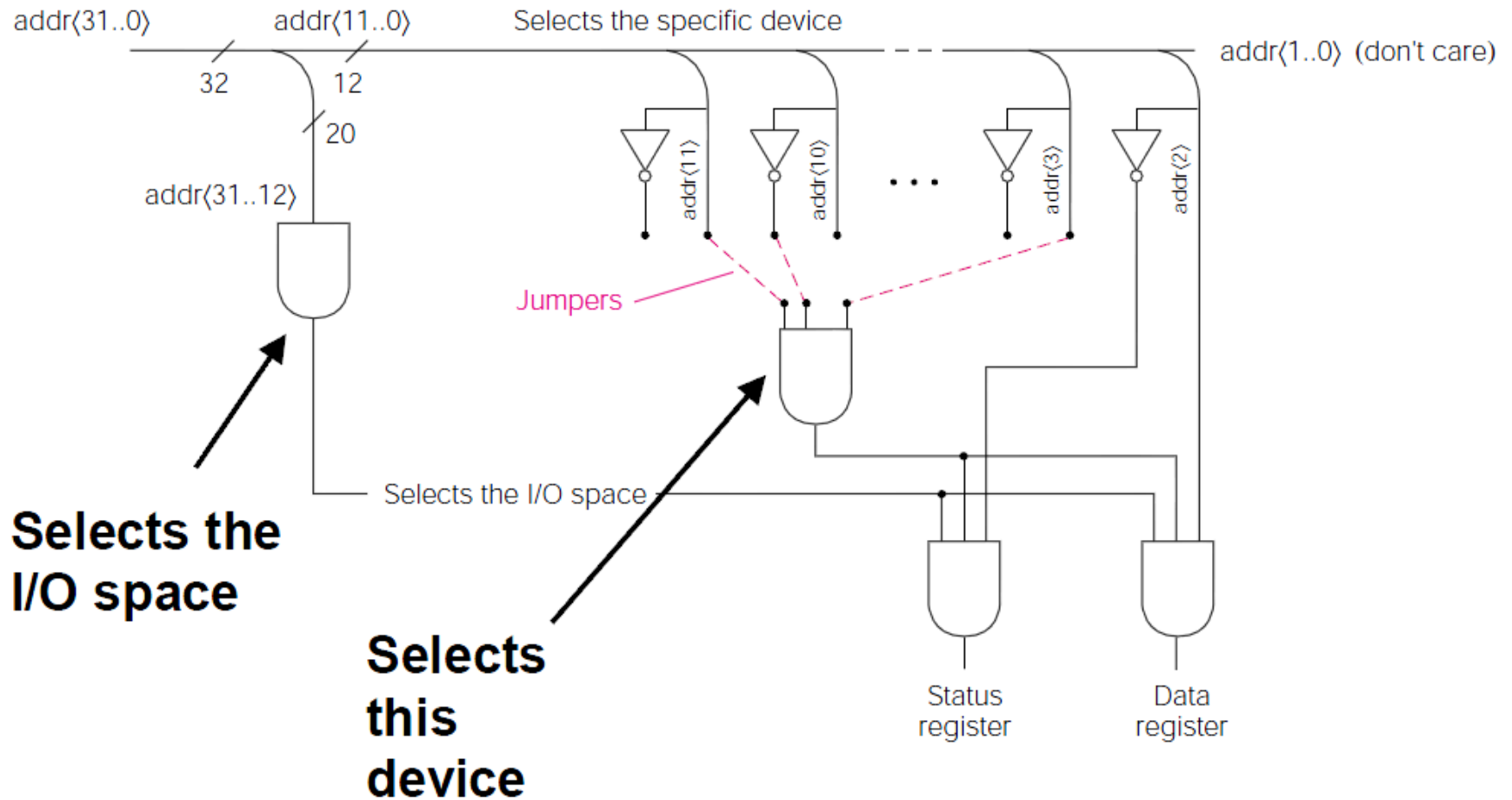

پایان

موفق و پیروز باشید