

LECTURE #14: RAM & ROM



EEL 3701: Digital Logic and Computer Systems

Based on lecture notes by Dr. Eric M. Schwartz

RAM = “Random Access Memory”

Static RAM (SRAM):

  - SRAM is *volatile*, meaning that it only retains data while the power is on.
- Typical access times for CMOS based SRAM are around 10ns-100ns
 - Other types of SRAM types are available
- Memory can be viewed as a *vector of registers*
- Each register is indexed by an *address* (a number, usually in hexadecimal).



- Memory volume terminology:

8 bits = 1 byte, 4 bits = 1 nibble,
 $2^{10} = 1024 = \text{“1K”}$ (kilo-), $2^{20} = \text{“1M”}$ (mega-),
 $2^{30} = \text{“1G”}$ (giga-), $2^{40} = \text{“1T”}$ (tera-)

- Memory requires n address lines, where 2^n is the number of memory addresses.
- Usually, the number of output lines is the same as the word size.
- Data lines are usually bi-directional (time-multiplexed)
 - Serve as an input when the “Write” state is True
 - Serve as an output when the “Read” state is True

Example: A 1KB RAM with an 8 bit word size (see figure above) requires:


10 address lines (A_9-A_0)

8 data lines (D_7-D_0)

Some control lines:

Chip Select (CS), Chip Enable (CE), Write Enable (WE),
 Read (RD), Output Enable (OE), etc.

Example: A 4 x 8 (4-Byte) SRAM:

 


(The following assumes that CS is True.)

- What output do we get if we “Read” A₁ = 0 and A₀ = 1? (42)₁₆
- How can we change (CA)₁₆ to (F1)₁₆?
 - Pull Read/Write low and introduce (F1)₁₆ on the data bus.

 Example: Construct a 512 x 8 memory module from two 256 x 8 SRAM’s.


The module should be wired to interface with a microprocessor that has 10 address lines, 8 data bits, and the necessary control bits.



**Address Wiring Diagram Combining Two
256-Byte Memories into a 512-Byte Memory**

- Where in memory are these located?
Answer: \$300-\$3FF and \$200-\$2FF
(Note: Symbols: \$ => Hexadecimal, @ => Octal, % => Binary)
- How could we move them from “high” memory to “low” memory?
 - On the first, swap the NAND for an OR.
 - On the second, move the NOT gate from A₈ to A₉.
- Could you mix around the address lines?
 - Yes, but the data wouldn’t be contiguous with normal addressing.

 - Sometimes RAM is organized like a matrix internally:



- How many address lines would this RAM require?
12, 3 for the columns and 9 for the rows.
- Does the internal arrangement matter to the user?
No. The inputs and outputs work the same.

Dynamic RAM (DRAM):

- DRAM is also *volatile* RAM.
- Uses RAS and CAS (Row/Column Address Select)
 - Always uses a matrix architecture.
- Row/Column addressing are time-multiplexed on the same address lines.

PRO:

- 1) Higher data density than SRAM (more data in less area = less cost)
 - 16MB (2^{24}) and even larger
- 2) Faster access time than SRAM

CON:

- 1) Must be periodically refreshed (re-written) or the data will be lost.


Read Only Memory (ROM):

- ROM is *non-volatile*, meaning that the data is saved even without power.
- ROM cannot be changed “on the fly.”

Types of ROM:

- ROM (masked ROM): Set by manufacturer. Cannot be modified.
- PROM (Programmable ROM): You program once by blowing fuses.
- EPROM (Erasable PROM): Reprogrammable. Erase using UV light.
- EEPROM (Electrically EPROM): Erased with voltage pulses.
- FLASH EEPROM: Newer and cheaper than standard EEPROM
 - Example: USB Flash Drives

 - ROM is used for storing unchanging software
 - i.e. Bootstraps for startup, BIOS (Basic I/O Services), etc.




Note: There is no “Write Enable” input. Poorly written software may attempt to write to ROM. Without precautions, this would cause a data collision on the bus (outputs connected together). To prevent this problem, hardware should include the “Read” signal (or NOT “Write”) as part of the criteria for enabling ROM.

Implementing a Truth Table with Memory:

TruthTable

A	B	C	X	Y	Z
0	0	0	1	1	0
0	0	1	0	1	1
0	1	0	0	1	0
0	1	1	1	0	1
1	0	0	0	0	1
1	0	1	0	0	0
1	1	0	1	1	1
1	1	1	1	0	0

 

- Inputs are connected to the address lines (i.e. A_2 , A_1 , and A_0).
 - These look up a byte in memory, whose values become the output.
- Extra address lines (i.e. A_3) can be tied high or low.
 - This effects which part of the memory is used, but not the operations.
- Internally, the Truth Table output values are stored.
 - The outputs are the LSb's of the byte at the corresponding address.
 - Ex. Address 1000 should contain xxxxx110 (see Truth Table above).